

Design and Functional Verification of a 32-bit ALU Using Verilog

Objectives: The objective of this project is to design and verify a 32-bit ALU in Verilog that performs arithmetic, logic, and shift operations. A functional testbench was used to check all commands and input combinations, including corner cases like divide-by-zero and underflow, ensuring the correct 64-bit outputs and proper tri-state behaviour.

Key Components of 32-bit ALU Project

1. ALU RTL Module (alu_32bit)

- Implements **32-bit arithmetic operations**: ADD, SUB, INC, DEC, MUL, DIV
- Implements **logical operations**: AND, OR, XOR, XNOR, INV, NAND, NOR, BUF
- Implements **shift operations**: SHL (shift left), SHR (shift right)
- Produces **64-bit output**
- Supports **tri-state output** with enable (oe)

2. Testbench (alu_32bit_tb)

- Drives **all input combinations** for operands a and b
- Iterates through **all 16 ALU commands**
- Controls **output enable** to test tri-state functionality
- Uses \$monitor to display **live outputs for verification**

3. Tasks for Reusability

- initialize → Reset all inputs
- inputs → Apply operands
- cmd → Set ALU command

- en_oe → Control output enable
- delay → Introduce simulation timing delays

4. Functional Verification

- Ensures **all operations produce correct outputs**
- Covers **corner cases**: divide by zero, underflow, inversion
- Validates **64-bit output results**

RTL

```

module alu_32bit (
    input [31:0] a_in,
    input [31:0] b_in,
    input [3:0] command_in,
    input      oe,
    output [63:0] d_out
);
    // ALU operation codes
    parameter ADD = 4'b0000, // Add a and b
           INC  = 4'b0001, // Increment a
           SUB  = 4'b0010, // Subtract b from a
           DEC  = 4'b0011, // Decrement a
           MUL  = 4'b0100, // Multiply a and b
           DIV  = 4'b0101, // Divide a by b
           SHL  = 4'b0110, // Shift left
           SHR  = 4'b0111, // Shift right
           AND  = 4'b1000, // AND
           OR   = 4'b1001, // OR
           INV  = 4'b1010, // Invert a
           NAND = 4'b1011, // NAND
           NOR  = 4'b1100, // NOR
           XOR  = 4'b1101, // XOR
           XNOR = 4'b1110, // XNOR
           BUF  = 4'b1111; // Buffer

    // Internal register
    reg [63:0] out;
    // Combinational logic
    always @(*) begin
        case (command_in)
    
```

```

    ADD : out = a_in + b_in;
    INC : out = a_in + 1;
    SUB : out = a_in - b_in;
    DEC : out = a_in - 1;
    MUL : out = a_in * b_in;
    DIV : out = (b_in != 0) ? a_in / b_in : 64'd0;
    SHL : out = a_in << 1;
    SHR : out = a_in >> 1;
    AND : out = a_in & b_in;
    OR  : out = a_in | b_in;
    INV : out = ~a_in;
    NAND : out = ~(a_in & b_in);
    NOR : out = ~(a_in | b_in);
    XOR : out = a_in ^ b_in;
    XNOR : out = ~(a_in ^ b_in);
    BUF : out = a_in;
    default : out = 64'd0;
endcase
end
// Tri-state output
assign d_out = oe ? out : 64'hZZZZ_ZZZZ_ZZZZ_ZZZZ;
endmodule

```

Testbench

```

`timescale 1ns/1ps
module alu_32bit_tb();
    // Testbench global variables
    reg [31:0] a, b;
    reg [3:0] command;
    reg enable;
    wire [63:0] out;

    // Variables for iteration of the loops
    integer m, n, o;

    // Parameter constants
    parameter ADD = 4'b0000,
              INC = 4'b0001,
              SUB = 4'b0010,
              DEC = 4'b0011,
              MUL = 4'b0100,
              DIV = 4'b0101,

```

```
SHL = 4'b0110,  
SHR = 4'b0111,  
AND = 4'b1000,  
OR  = 4'b1001,  
INV = 4'b1010,  
NAND = 4'b1011,  
NOR = 4'b1100,  
XOR = 4'b1101,  
XNOR = 4'b1110,  
BUF = 4'b1111;
```

```
// String for displaying command  
reg [8*5:0] string_cmd;
```

```
// Step1 : Instantiate the DUT
```

```
alu_32bit dut (  
    .a_in(a),  
    .b_in(b),  
    .command_in(command),  
    .oe(enable),  
    .d_out(out)  
);
```

```
// Step2 : Initialize task
```

```
task initialize;  
    begin  
        {a, b, enable, command} = 0;  
        #10;  
    end  
endtask
```

```
// Enable task
```

```
task en_oe(input i);  
    begin  
        enable = i;  
    end  
endtask
```

```
// Input task
```

```
task inputs(input [31:0] j, k);  
    begin  
        a = j;  
        b = k;  
    end  
endtask
```

```
end  
endtask
```

// Command task

```
task cmd(input [3:0] l);  
begin  
    command = l;  
end  
endtask
```

// Delay task

```
task delay;  
begin  
    #10;  
end  
endtask
```

// Command string decoding

```
always @(command) begin  
    case (command)  
        ADD : string_cmd = "ADD";  
        INC : string_cmd = "INC";  
        SUB : string_cmd = "SUB";  
        DEC : string_cmd = "DEC";  
        MUL : string_cmd = "MUL";  
        DIV : string_cmd = "DIV";  
        SHL : string_cmd = "SHL";  
        SHR : string_cmd = "SHR";  
        AND : string_cmd = "AND";  
        OR  : string_cmd = "OR";  
        INV : string_cmd = "INV";  
        NAND : string_cmd = "NAND";  
        NOR : string_cmd = "NOR";  
        XOR : string_cmd = "XOR";  
        XNOR : string_cmd = "XNOR";  
        BUF : string_cmd = "BUF";  
        default: string_cmd = "UNK";  
    endcase  
end
```

// Stimulus generation

```
initial begin  
    initialize;
```

```

en_oe(1'b1);

for (m = 0; m < 16; m = m + 1) begin
    for (n = 0; n < 16; n = n + 1) begin
        inputs(m, n);
        for (o = 0; o < 16; o = o + 1) begin
            command = o;
            delay;
        end
    end
end

// Tri-state test
en_oe(0);
inputs(32'd20, 32'd10);
cmd(ADD);
delay;

en_oe(1);
inputs(32'd25, 32'd17);
cmd(ADD);
delay;


$finish;
end

// Monitor output
initial begin
    $monitor("oe=%b a=%d b=%d cmd=%s out=%d",
        enable, a, b, string_cmd, out);
end


endmodule

```


Top – Level Block

 

Schematic View

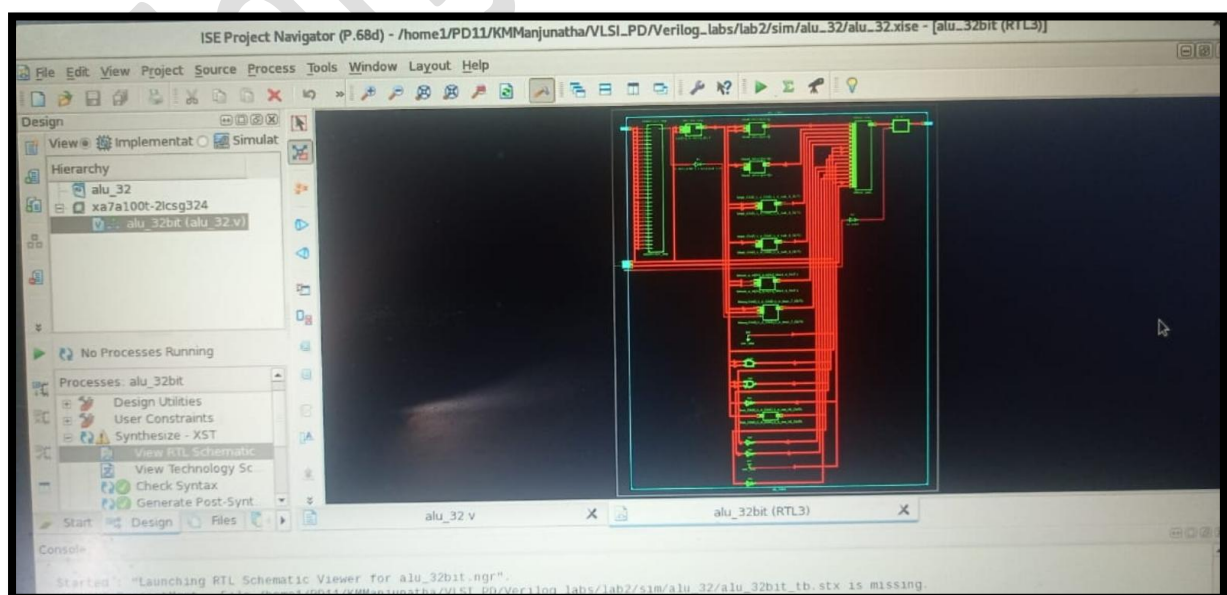

Simulation

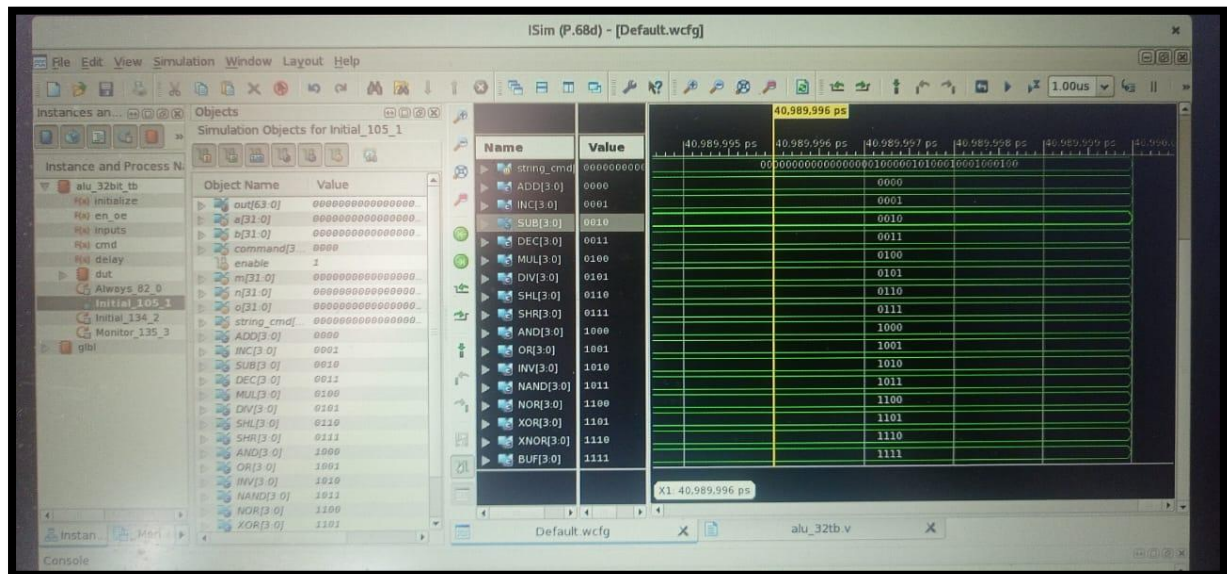

Console Window Output

```
Console
oe=1 a= 15 b= 14 cmd= MUL out= 210
oe=1 a= 15 b= 14 cmd= DIV out= 1
oe=1 a= 15 b= 14 cmd= SHL out= 30
oe=1 a= 15 b= 14 cmd= SHR out= 7
oe=1 a= 15 b= 14 cmd= AND out= 14
oe=1 a= 15 b= 14 cmd= OR out= 15
oe=1 a= 15 b= 14 cmd= INV out=18446744073709551600
oe=1 a= 15 b= 14 cmd= NAND out=18446744073709551601
oe=1 a= 15 b= 14 cmd= NOR out=18446744073709551600
oe=1 a= 15 b= 14 cmd= XOR out= 1
oe=1 a= 15 b= 14 cmd= XNOR out=18446744073709551614
oe=1 a= 15 b= 14 cmd= BUF out= 15
oe=1 a= 15 b= 15 cmd= ADD out= 30
oe=1 a= 15 b= 15 cmd= INC out= 16
oe=1 a= 15 b= 15 cmd= SUB out= 0
oe=1 a= 15 b= 15 cmd= DEC out= 14
oe=1 a= 15 b= 15 cmd= MUL out= 225
oe=1 a= 15 b= 15 cmd= DIV out= 1
oe=1 a= 15 b= 15 cmd= SHL out= 30
oe=1 a= 15 b= 15 cmd= SHR out= 7
```